

**Aim:** To familiarize with active and passive electronic components.

→ **Apparatus required:-**

Resistors (Various values), Capacitors (Ceramic, electrolytic), Inductors, Diode, LED, Transistors, Breadboard, Connecting wires, multimeter, power supply/Battery.

→ **Theory :-** Electronic components are classified into two types:

**Passive Components:** These components do not require power to operate and do not amplify signals.

Example:

Electronic components

Resistor → limits current flow.

Capacitor → Stores electrical energy.

Inductor → stores energy in a magnetic field.


**Active Components :**

These components require an external source of energy and can amplify signals.

Eg. Diode - Allows current to flow in one direction only.

AJAYA

### Resistor:

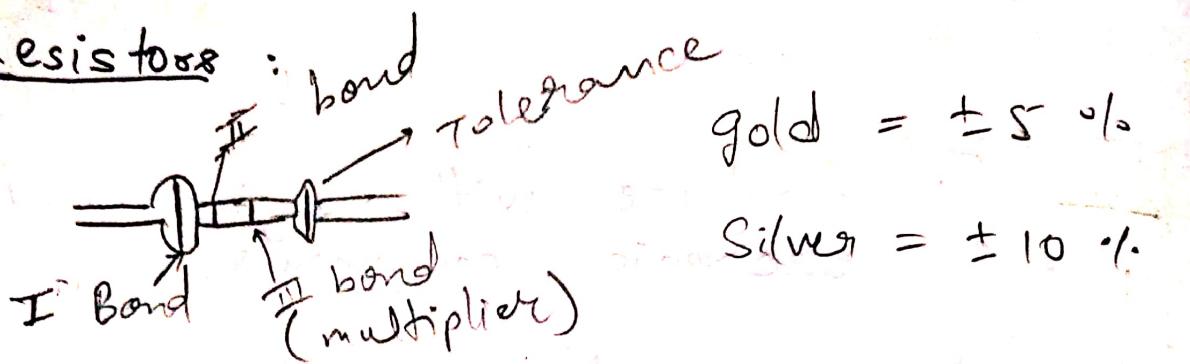


gold =  $\pm 5\%$

Silver =  $\pm 10\%$


### Capacitor:




### Transformer:

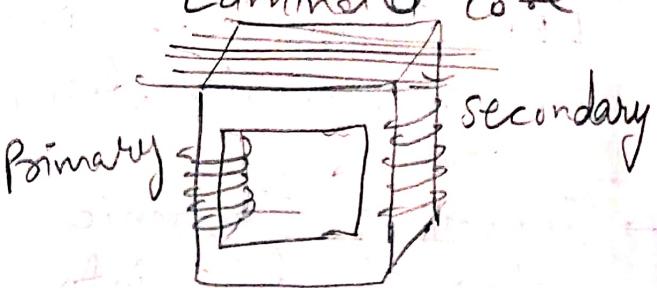

### Inductor:

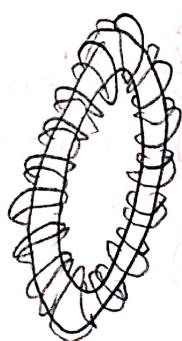

(silicon transistors)

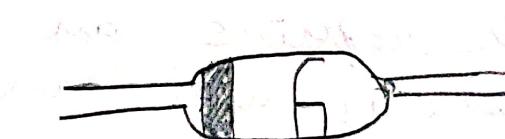

Silicon diodes

(Zener diode)

- LED (light emitting Diode) - Emits light when forward biased.
- Transistor Acts as a switch or amplifier.

### Procedure :-

1. Resistors :- Observe physical appearance Read colour codes to find resistance value. Verify value using a multimeter.

2. Capacitors :- Observe ceramic and electrolytic types. Note polarity in electrolytic capacitors. Measure capacitance (i.e LCR meter available)

3. Inductors :- Observe wire-wound structure Identify rating (if possible) pointed) ~~Diagnose~~

4. Diodes :- identify cathode (marked with a silver band). Test with multimeter in diode mode

### 5. LEDs

Observe polarity : long leg is anode .

Connect in series with resistor and apply voltage to test lighting.

Transistor :- Identify the pins (Emitter, Base, Collector) using datasheet.

Test using multimeter in diode mode.

### Observation :-

<u>Components</u>	<u>Symbol</u>	<u>function</u>
• Resistor	R	limits current
• Capacitor	C	stores electric charge.
• Inductor	L	stores magnetic energy.
• Diode	D	Allows unidirectional current
• LED	-	Emits light
• Transistor	Q	Acts as switch /amplifier

Result :- The active and passive components were successfully identified and tested. Their characteristics and functions


AJAYA

were understood.

Conclusion:- The practical provided hands-on experience with basic electronic components, helping to understand their physical appearance, identification, and usage in circuits.

B  
17/8/15

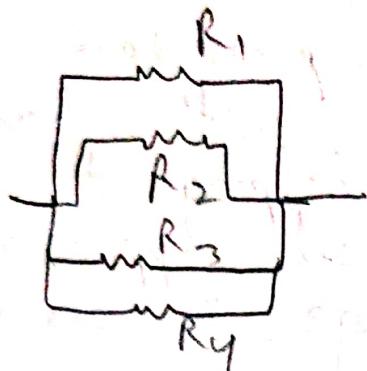$R_1 \parallel R_2 \parallel R_3 \parallel R_4$   $\rightarrow$  Series Connection



$R_1 \parallel R_2 \parallel R_3 \parallel R_4$   $\rightarrow$  Parallel Connection

	1, 2 Band	Multiply by:
Black	0	$\times 1$

Brown	1	$\times 10$
-------	---	-------------

Red	2	$\times 100$
-----	---	--------------

Orange	3	$\times 1k$
--------	---	-------------

Yellow	4	$\times 10k$
--------	---	--------------

Green	5	$\times 100k$
-------	---	---------------

Blue	6	$\times 1M$
------	---	-------------

Violet	7	$\times 10M$
--------	---	--------------

Grey	8	$\times 100M$
------	---	---------------

White	9	$\times 1G$
-------	---	-------------

Aim: To study and understand the behaviour of resistors, bulbs or other components when connected in series & parallel circuits.

→ Apparatus required:

- DC power supply / Battery (5V - 12V)
- Resistors, connecting wires, Breadboard.
- Multimeter, switch, Ammeter, Voltmeter.

→ Theory :-

① Series connection : Components are connected end-to-end forming a single path for current.

Current is same through all components.

• Total resistance :

$$R_{\text{total}} = R_1 + R_2 + R_3 + \dots$$

voltage divides across each resistors based on resistance.

② Parallel Connection : Components are connected across the same two points, forming multiple paths for current. Voltage is same across all components.

(1)

$R_1$   $R_2$   $R_3$

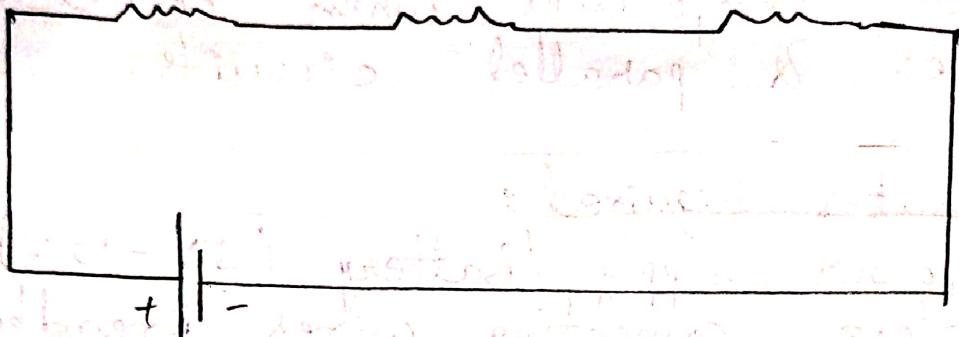


fig - Series Circuit

(2)

$R_1$

$R_2$

$R_3$

Electrode



fig - parallel circuit

Total resistance :

$$\frac{1}{R_{\text{total}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

Current divides across each path.

→ Procedure :-

### A) Series Connection :


- ① Connect three resistors in series on the breadboard.
- ② Connect power supply and ammeter in series with the circuit.
- ③ Measure the total current using the ammeter.
- ④ measure the voltage across each resistor using a voltmeter.
- ⑤ Note down the values.

### B) Parallel Connection :

- ① Connect the same 3 resistors in parallel on the Breadboard.

## Calculation :



①

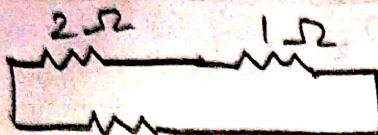

$$\frac{1}{R_{eq}} = \frac{1}{3} + \frac{1}{2} \Rightarrow \frac{2+3}{6} = \frac{5}{6}$$

$$R_{eq} = \frac{6}{5} \Omega$$

②

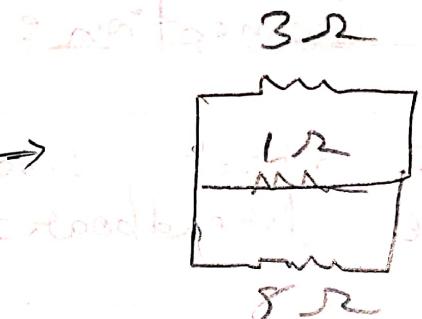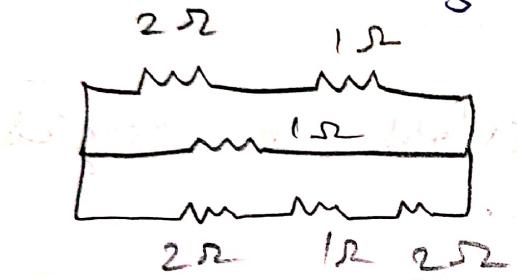

$$\frac{1}{R_{eq}} = \frac{1}{3} + \frac{1}{1} + \frac{1}{2} = \frac{8+15+3}{18}$$

$$\frac{1}{R_{eq}} = \frac{23}{18}$$

$$R_{eq} = \frac{18}{23}$$

- (2) Connect the power supply and ammeter in series before the junction.
- (3) Measure the total current and individual branch currents.
- (4) Measure the voltage across each resistor.
- (5) Note down the values.

Observations :-

Connection type

Series

Resistor values

$R_1, R_2, R_3$

Parallel

$R_1, R_2, R_3$

Connection type

Total resistance

Series

$$R_{\text{total}} = R_1 + R_2 + R_3$$

Parallel

$$\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Calculations:

Calculate theoretical values of total resistance for both cases.

AJAYA

→ verify ohm's law :  $V = IR$ .

• Result → In a series circuit, current remains constant while voltage divides across resistors.

→ In a parallel circuit, voltage remains constant while current divides across branches.

practical values matched closely with theoretical calculations.

### Precautions :

- ① Check all connections properly before switching on the power.
- ② Use resistors of suitable rating to prevent overheating.
- ③ Ensure correct polarity of meters and power supply.
- ④ Do not touch open wires while the circuit is powered.

→ Conclusion: The experiment helped us to clearly understand the difference b/w series & parallel circuits. It also validated ohm's law and taught how to calculate total resistance in different connections.

AJAYA

Teacher's Signature

Rohit Singh